

## APPLICATION NOTE

**AN 147** 

FAN FAILURE SAFETY LOCK-OUT CIRCUIT

The use of a safety lock-out circuit is highly recommended. The circuit below is effective at stopping the humidifier operation if the fan motor fails for any reason. The use of a system interlock is optional and not required for basic operation. Failure to incorporate a lock-out can result in excessive condensation inside the duct work and/or possible flood damage, if the HVAC Fan/Blower fails to operate. This solution is provided as a supplement. Flood or water damage as a result of not using this diagram is not the responsibility of EWC Controls Inc.

## FAN FAILURE SAFETY LOCK-OUT CIRCUIT

